

**Royal College of Arts Science and Commerce**  
**TYBSc Physics**  
**Semester: VI**  
**Paper:II – Electronics**  
**Sample Questions**

1.	The common-source JFET amplifier has .....
a	a very high input impedance and a relatively low voltage gain
b	a high input impedance and a very high voltage gain
c	a high input impedance and a voltage gain less than 1
d	no voltage gain
2.	Which type of JFET bias requires a negative supply voltage?
a	feedback
b	source
c	gate
d	Voltage divider
3.	In the constant-current region, how will the $I_{DS}$ change in an n-channel JFET?
a	As $V_{GS}$ decreases $I_D$ decreases.
b	As $V_{GS}$ increases $I_D$ decreases
c	As $V_{GS}$ decreases $I_D$ remains constant.
d	As $I_D$ increases $V_{GS}$ remains constant.
4.	A MOSFET has _____ terminals.
a	two
b	Five
c	Four
d	Three
5.	Which of the following devices has the highest input impedance?
a	JFET
b	MOSFET
c	crystal diode
d	ordinary transistor
6.	In a MOSFET, the metal area of the gate, along with the insulating dielectric oxide layer and the semiconductor channel, forms a _____.
a	bipolar junction transistor
b	resistive network
c	parallel plate capacitor
d	Unipolar junction transistor
7.	An SCR has ..... p n semiconductor
a	One
b	Two
c	Three
d	Four

8	FOR gate open in SCR current does not flows through load resistance , due to junction ----- and -----.
a	J1,J2 forward bias j3 reverse bias
b	J1,J3 forward bias j2 reverse bias
c	J3,J2 forward bias j1 reverse bias
d	J1 forward bias j2,j3 reverse bias
9	Differential amplifier operates at----- Voltage.
a	At high Voltage (~ 100 KV).
b	At medium voltage (~230 V).
c	At Low Voltage (~ 12V).
d	At very low voltage (~ 12 mV).
10	The following is not the property of OPAMP.
a	OPAMP is single stage amplifier.
b	A high input impedance.
c	A large open loop gain
d	Very large CMRR.
11.	A common – mode signal is applied to-----.
a	The noninverting input.
b	The inverting input.
c	Both inputs.
d	To top of tail resister.
12	In a voltage controlled current source with op-amp, the circuit acts like a
a	Voltage amplifier
b	Current – to - voltage source
c	Voltage –to-current source
d	Current amplifier
13	Instrumentation amplifier is extension of
a	Inverting amplifier
b	Non- Inverting amplifier
c	summing amplifier
d	Differential amplifier
14	When Transistor is saturated, it act like a closed switch between collector and _____.
a	Collector
b	Base
c	Emitter
d	Power supply
15	What is the function of the comparators in the 555 timer circuit?
a	to compare the output voltages to the internal voltage divider
b	to compare the input voltages to the internal voltage divider
c	to compare the output voltages to the external voltage divider
d	to compare the input voltages to the external voltage divider

16	_____ is added to the series regulator to protect pass transistor from excessive current or short circuit.
a	Short circuit
b	Voltage limiting circuit
c	Current limiting circuit
d	Open circuit
17	Ripple rejection of 80dB means that reduced the input ripple by a factor of _____
a	10000
b	1000
c	100
d	100000
18	A standard TTL gate has a power dissipation of about _____
a	10 milliwatts (mW).
b	20 milliwatts (mW).
c	30 milliwatts (mW).
d	40 milliwatts (mW)
19	In digital communication the cable acts like a .....which filters out the higher harmonics.
a	Low pass filter
b	high pass filter
c	band pass filter
d	Band stop filter
20	What is the output voltage if the input voltage of a compander with a maximum voltage range of 1 V and a $\mu$ of 255 is 0.25?
a	0.08V
b	0.75V
c	1.02V
d	1.54V